



IC_Project 2

Name	ID	Student Number
عبد الرحمن بدوي محمد	9220426	78
عاصم حسين محمد	9220419	76
يوسف خالد عمر محمود	9220984	170
عمر ايمن امين	9220528	90

-----Table of figures-----

Figure 1: Sizing Test Bench	2
Figure 2: Folded Cascode Operating Point	5
Figure 3: Bias Circuit.....	5
Figure 4 Final Circuit Test.....	6
Figure 5 AC-TEST	6
Figure 6 CMMR vs frequency	7
Figure 7 PSRR differential vs frequency	8
Figure 8 PSRR common vs frequency	8
Figure 9 Unity feedback circuit	9
Figure 10 STB TEST	9
Figure 11 STB TEST-OUTPUT.....	10
Figure 12 DC gain vs Vin DC	10
Figure 13 Closed Loop AC analysis	11
Figure 14 Top Noise Contributors.....	
Figure 15 Vout Transient Output	
Figure 16 Vout due to sin input	12
Figure 17 Vout Spectrum.....	13
Figure 18 Vout Impluse Response	13

Design Methodology :-

- Devices Used for the amplifier are nch_25od33 and pch_25od33 ,because Vdd = 3.3V which is high for regular nch and pch devices.

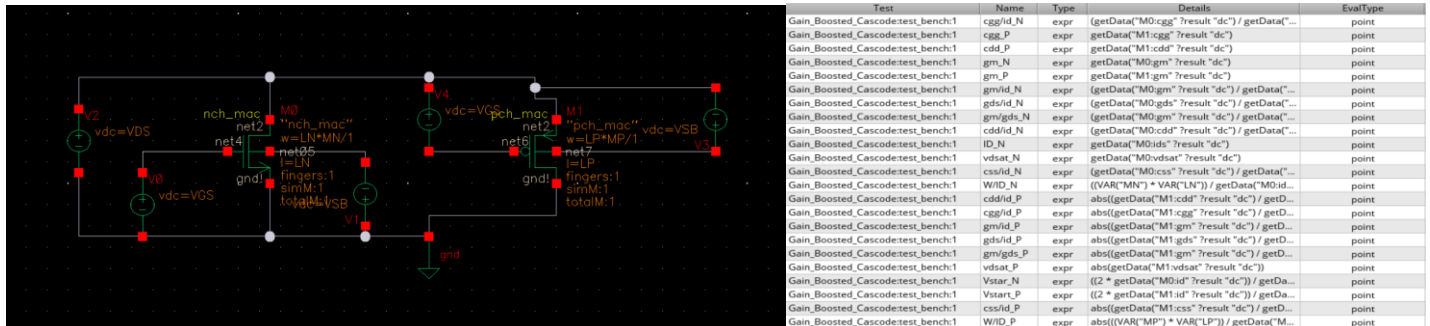


Figure 1: Sizing Test Bench

Folded Cascode Desing:-

 


Figure 1. Folded Cascode

The main design Equations for the Folded Cascode Amplifier are the following:

from the Slew Rate $SR = \frac{I_1}{C_L}$ Spec : form this spec it's follows that the minimum current for , To get the actual $I_1 = 100\mu A$ value of the current from GBW spec.

GBW (Taking Safty factor of 20% for parasitics),

$$\text{Choose } gm/id = 18 \text{ and } I_D = 65\mu A, \text{ meaning } I_{SS} = 130\mu A > 100\mu A = \frac{gm}{(C_L + C_{par}) 2\pi} \approx \frac{gm_{input}}{1.2 C_L}.$$

Since we are using the 3.3V devices L_{min} is quite high $L_{min} = 500n$ for NMOS and $400n$ for PMOS, and this achieves all the specs (Gain = 67dB >> 58dB), So we go with L_{min} for all devices except for tail current source ($L = 1\mu$).

 


Figure 2. Folded Cascode schematic with voltage assignment

Based ON VINCM spec and output swing , nominal voltages are assigned as in fig-2, For the current I3, it was first chosen to be $\frac{3}{4} I_1$ (meaning current ratio of 1/2 in the two branches).

Now , given currents, voltages and L , we can determine bias voltages and Widths for each transistor, For Bias Voltages: $V_{b1} = 2.54V$, $V_{b2} = 1.94V$, $V_{b3} = 1.35V$ and for tail source $V_{gs} = 0.65V$.

1.2 Bias Circuit

Now for the bias circuit:

 


Figure 3. Bias Circuit and Current Mirrors

- 1 **For the current in each branch** , it was done by experiment to get proper voltages with reasonable sizes of the transistor, it should be noted that for the optimum bias Vb2 , we intentionally chosen it to get a V_{ds} of 0.5V as making $V_{ds} = V_{ov} + 100\text{mv}$ degrade the performance a lot (Not only the gain but GBW and SR was badly affected) , so we choose to give it a larger marge $V_{ds} = 0.5\text{V}$. **1.3 Final Sizing:**
- 2 After running simulations, small changes was made to better achieve the specs, here the final sizing.

Device	W	L	Vgs
Input Pair	60u	500n	820mV
PMOS Source	28.36u	400n	760mV
PMOS cascode	10u	400n	860mV
NMOS cascode	10.15u	500n	850mV
NMOS CM	1.25u	500n	1V
NMOS Tail Source	110u	1u	650mV

Table 1. Sizing of Folded Cascode

Device	W	L	Vgs	Device	W	L	Vgs
M0	5.9u	400n	0.76	M1	5.9u	400n	0.76
M2	28.7u	1u	0.65	M3	14.35u	1u	0.65
M4	4.2u	400n	1.36	M5	1.21u	1u	1.36V
M6	7.2u	400n	0.76	M7	13.8u	500n	1.35
M8	740n	1u	1.35V				

Table 2. Sizing of Bias Circuit

2.1.1 DC Operating Points

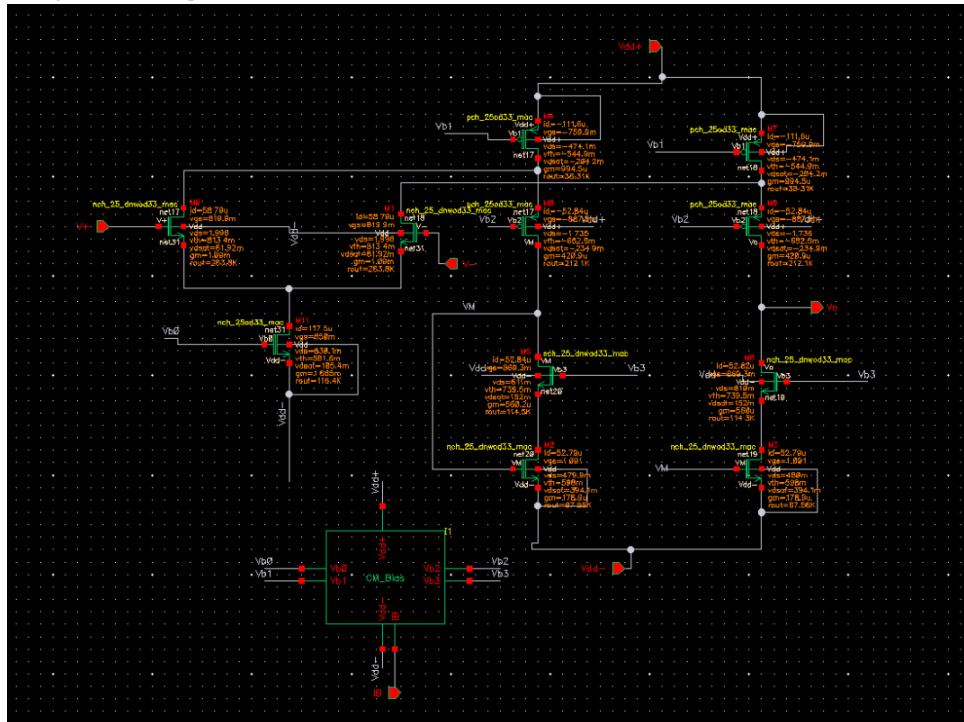


Figure 2: Folded Cascode Operating Point

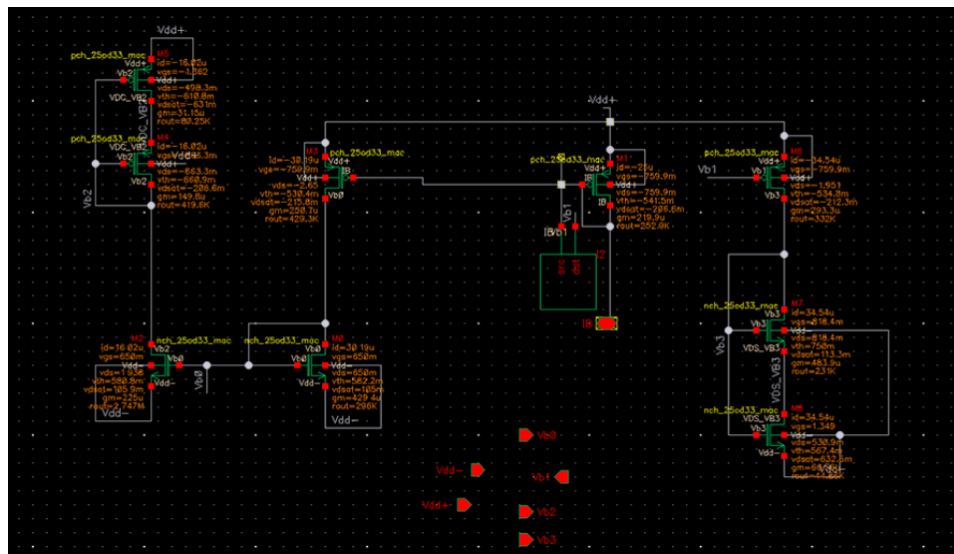


Figure 3: Bias Circuit

3 Simulation Test

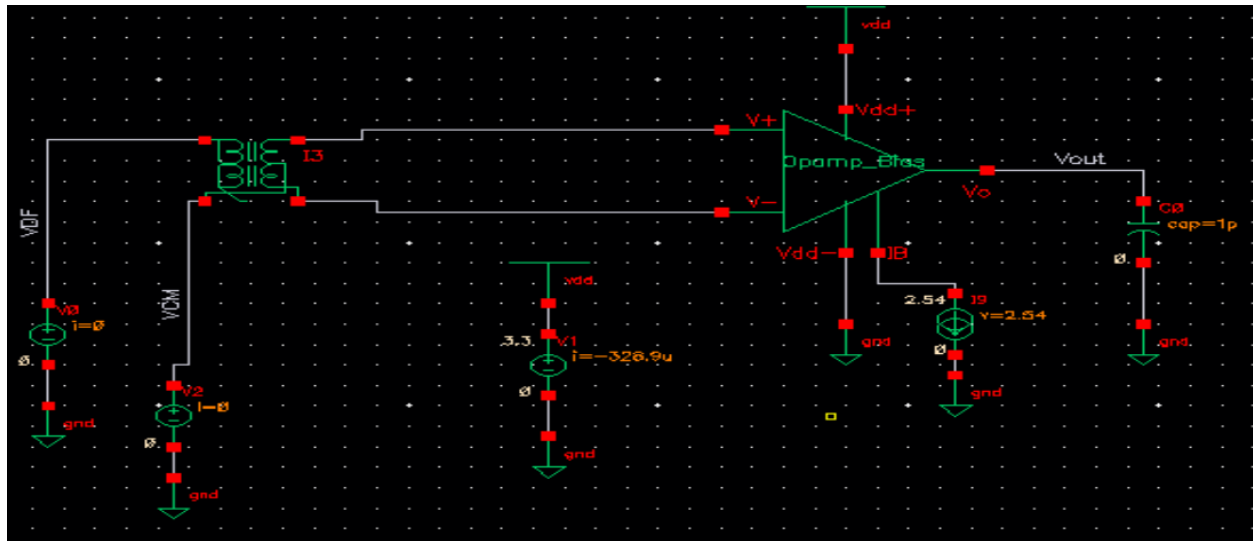


Figure 4 Final Circuit Test

3.1 Open Circuit Analysis:

We used ideal balun

3.1.1 ==> AC test

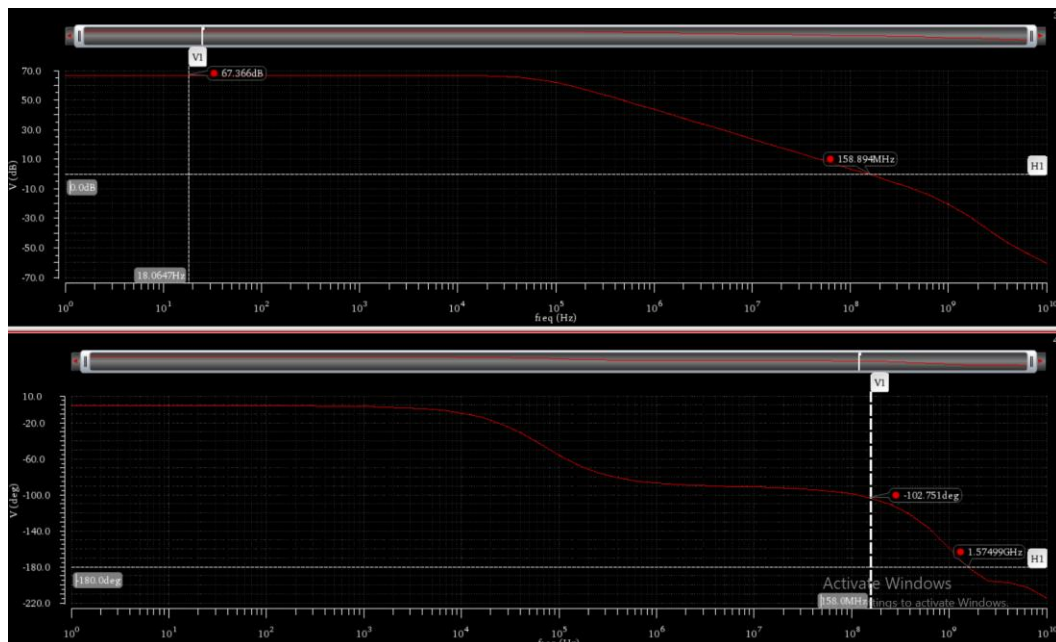


Figure 5 AC-TEST

As shown in figure 5, the Dc gain is 67.3 and the PM is $180 - 102.8 = 77.2$ with Gain Bandwidth = 163.2M

Expression	Value	Expression	Value
1 phaseMargin(...	77.19	gainBwProd(v(...	163.2E6

Hand analysis:

$$A_{vd} = g_{m1,2} * R_{out}$$

$$R_{out} = R_{up} // R_{down}$$

$$R_{up} = (r_{o1,2} // r_{o9,10}) * g_{m7,8} * r_{o7,8} = 3.9 \text{ Mohm}$$

$$R_{down} = r_{o3,4} * r_{o5,6} * g_{m5,6} = 3.18 \text{ Mohm}$$

$$R_{out} = 1.75 \text{ Mohm}$$

$$AVD = 66 \text{ dB}$$

$$G_{BW} \approx g_{m1,2} / (2\pi * CL) = 173 \text{ M}$$

Comment:

Theoretical GBW is **less than** simulated GBW

3.1.2 → XF test

 


Figure 6 CMRR vs frequency

As shown in figure 6, the CMRR is 102.232 dB

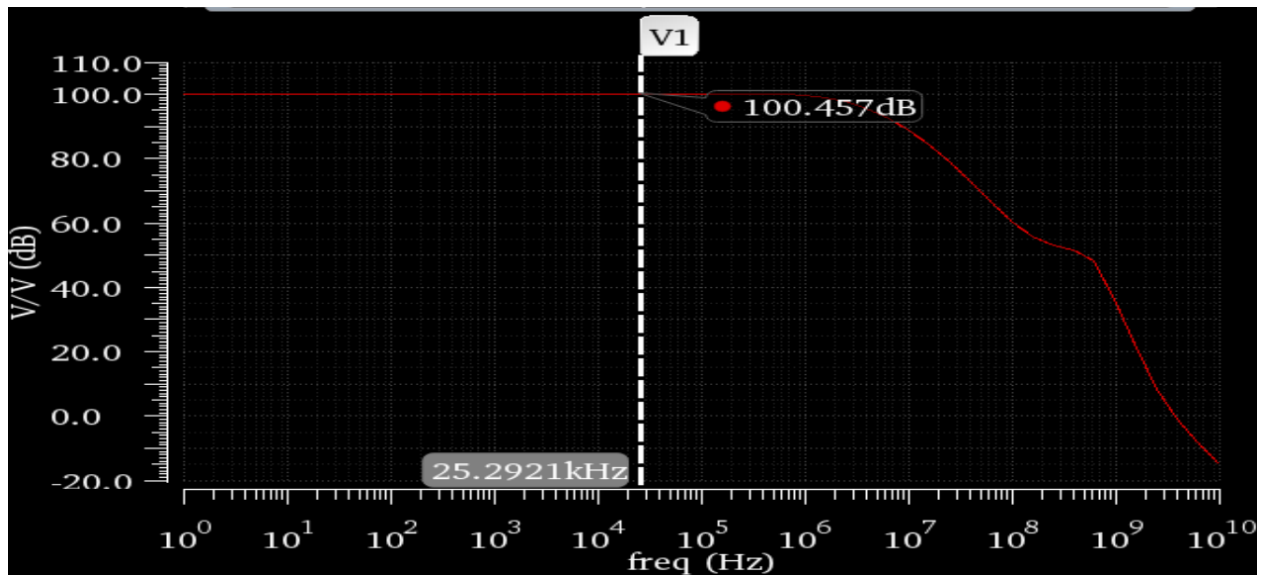


Figure 7 PSRR differential vs frequency

 


Figure 8 PSRR common vs frequency

As shown in figure 7 and figure 8, the PSRR differential is 100.457 dB while PSRR common is -1.7742 dB.

3.2 ==> Unity Closed loop Analysis:

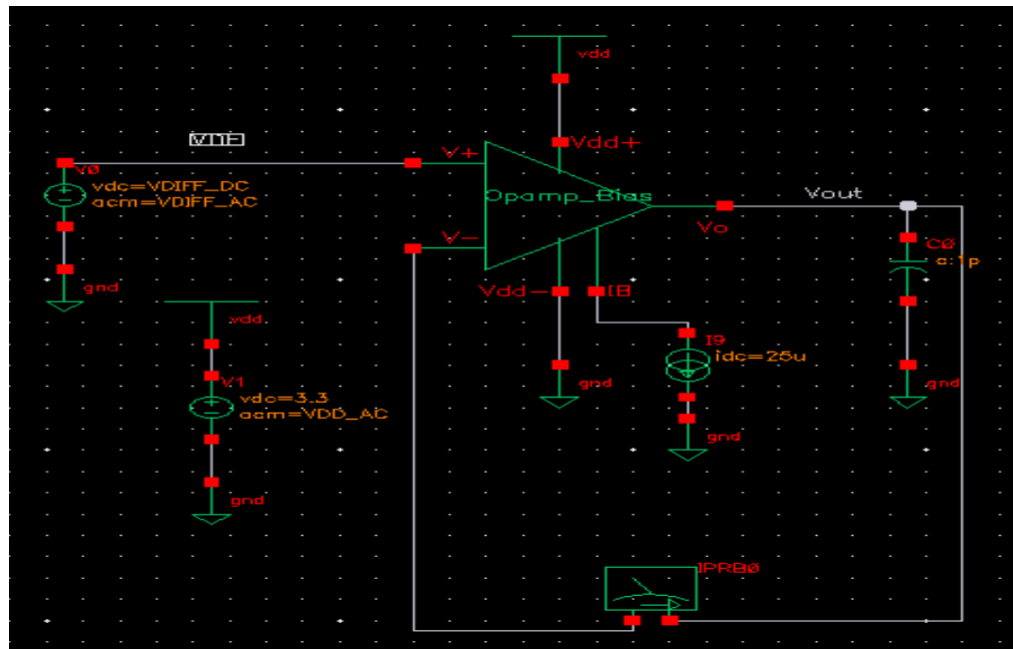


Figure 9 Unity feedback circuit

As shown in figure 10, We used Iprobe in the unity feedback.

3.2.1 → STB test

 


Figure 10 STB TEST

As shown in figure 10, the STB loop gain and phase is the same as the AC analysis.

	WB_VB3_CM	/phaseMargin (Deg)	/gainMargin (dB)	/gainMarginFreq (Hz) ^	/phase...q (Hz)
1	740.0E-9	78.26	29.70	1.707E9	144.9E6

Figure 11 STB TEST-OUTPUT

As shown in figure 11, the Gain margin is 29.7 dB with $W_{gc} = 1.71 \text{ GHz}$ and Phase Margin is 78.26 with $W_{pm} = 144.9 \text{ MHz}$

Comment:

GBW is **less than** the AC open loop simulation as load capacitance is added with the input pair capacitance

In AC Open Loop:

PM = 77.2 with Gain Bandwidth = 163.2M

3.2.2 ==> DC-gain Analysis:

 


Figure 12 DC gain vs Vin DC

As shown in figure 12, The input range is between 760m and 2.48 which is **bigger than 1.5 VPP**.

3.2.3 AC Analysis:

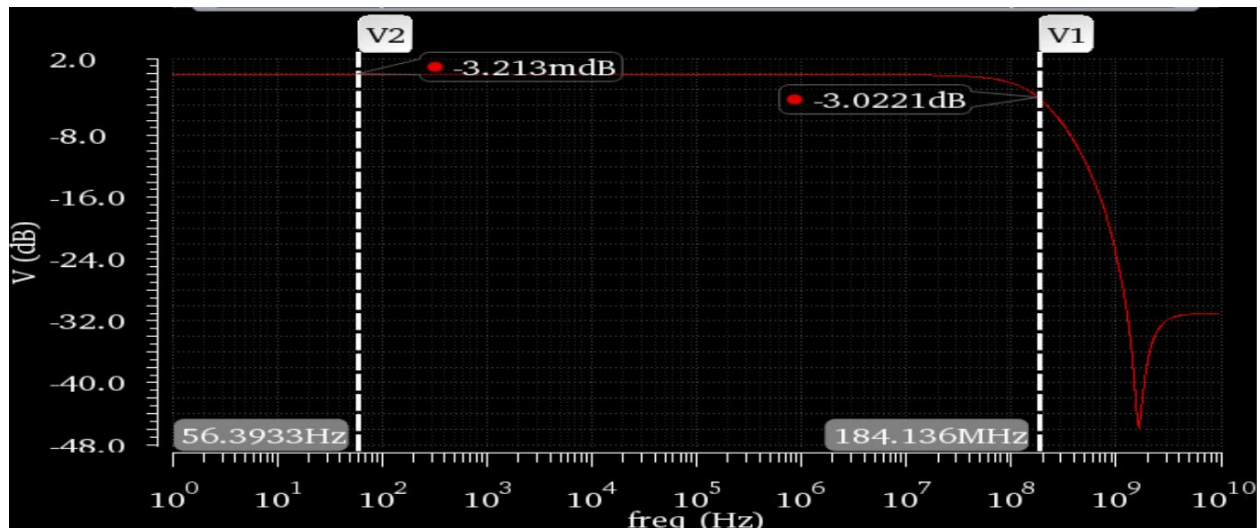


Figure 13 Closed Loop AC analysis

As shown in figure 13, the $A_{cl} = -3.23$ m dB with $BW = 184.1$ MHz

Comments:

BW is **larger than** GBW as operating point is different from open loop.

Gain of closed loop is less than 0 dB.

Gain of open loop is finite.

3.2.4 Noise Analysis:

Device	Param	Noise Contribution	% Of Total
/I2/M4	id	3.42435e-09	23.46
/I2/M7	id	3.41726e-09	23.37
/I2/M1	id	3.14741e-09	19.82
/I2/M0	id	3.14407e-09	19.78
/I2/M3	id	1.51658e-09	4.60
/I2/M2	id	1.51626e-09	4.60
/I2/M3	fn	8.04967e-10	1.30
/I2/M2	fn	8.01352e-10	1.28

Spot Noise Summary (in V/sqrt(Hz)) at 10M Hz Sorted By Noise Contributors
Total Summarized Noise = 7.06945e-09
Total Input Referred Noise = 7.08131e-09

Figure 14 Top Noise Contributors

As shown in figure 14, the top 4 contributors @10MHz are M4, M7, M1 and M0 with total noise = 7.08 nV/Hz < 10 nV/Hz.

Comment:

Cascode doesn't contribute to the noise as cascode devices see generated gain. Most Noise contributors are input pair and PMOS Current source at folding node.

3.2.5 Transient Analysis:

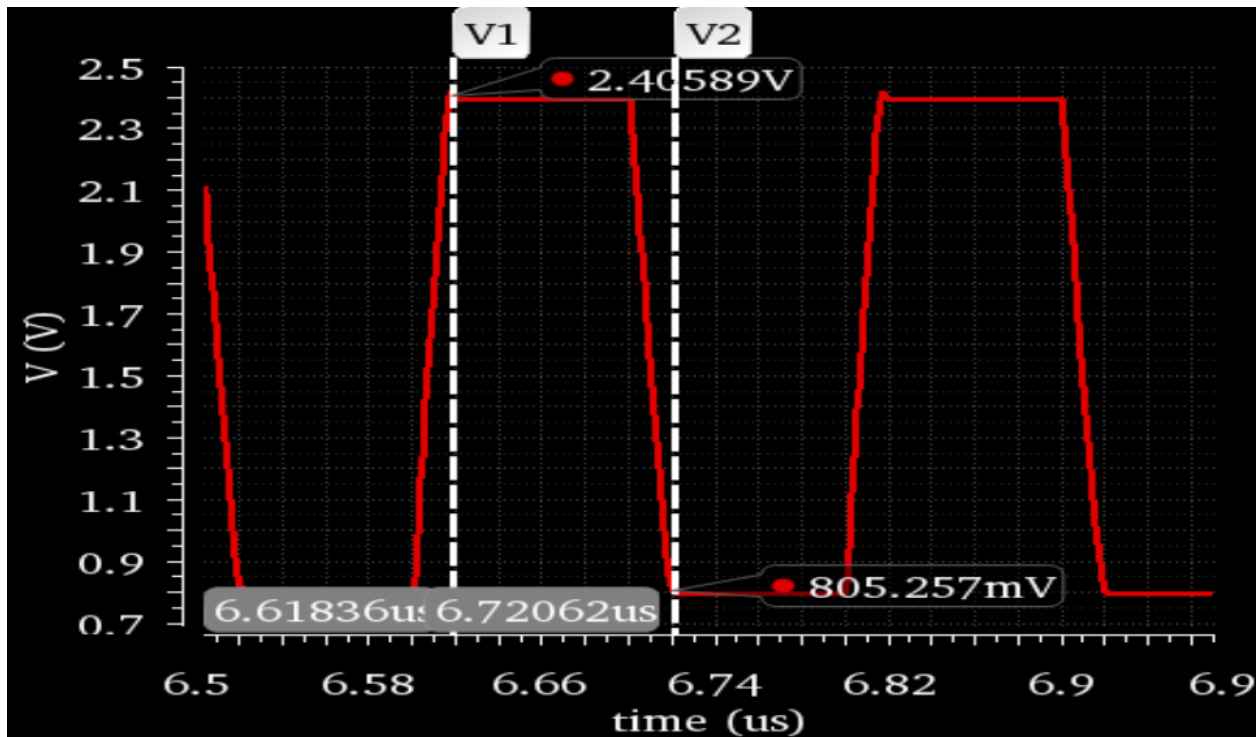


Figure 15 Vout Transient Output

As shown in figure 16, The Slew Rate $SR = \frac{2.405 - 0.805}{6.7206 - 6.618} \approx 105M$

3.2.6 → Spectrum Analysis:

 


Figure 16 Vout due to sin input

As shown in figure 16, the output is not pure sine wave.

folded_cascode:Closed_Loop_TB:1	SR	102.6M
---------------------------------	----	--------

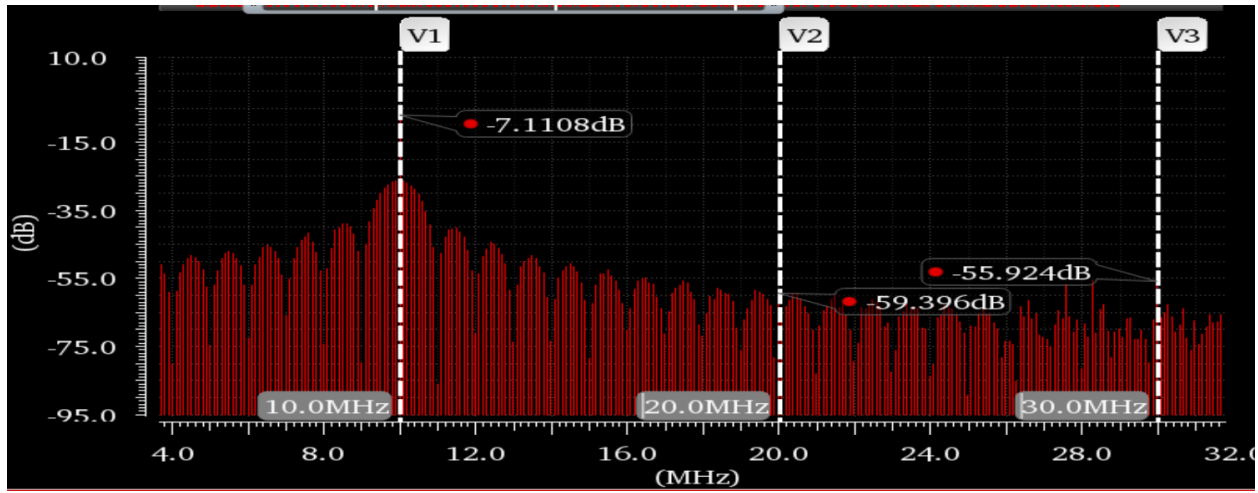


Figure 17 Vout Spectrum

As shown in figure 17, The $HD2 = 20 \cdot \log_{10} \left(\frac{V_{2\omega}}{V_{\omega}} \right) = -59.39 + 7.11 = -52.28 \text{ dB}$

And $HD3 = 20 \cdot \log_{10} \left(\frac{V_{3\omega}}{V_{\omega}} \right) = -55.92 + 7.11 = -48.81 \text{ dB}$

As for the all harmonics:

folded_cascode:Closed_Loop_TB:1	spectrum_totalharmpower	-52.47
folded_cascode:Closed_Loop_TB:1	spectrum_dcpower	4.352
folded_cascode:Closed_Loop_TB:1	spectrum_thddb	-45.36
folded_cascode:Closed_Loop_TB:1	spectrum_thd	539.4m
folded_cascode:Closed_Loop_TB:1	spectrum_snr	9.469

THD = -45.36 dB = 0.539%

Error Analysis:

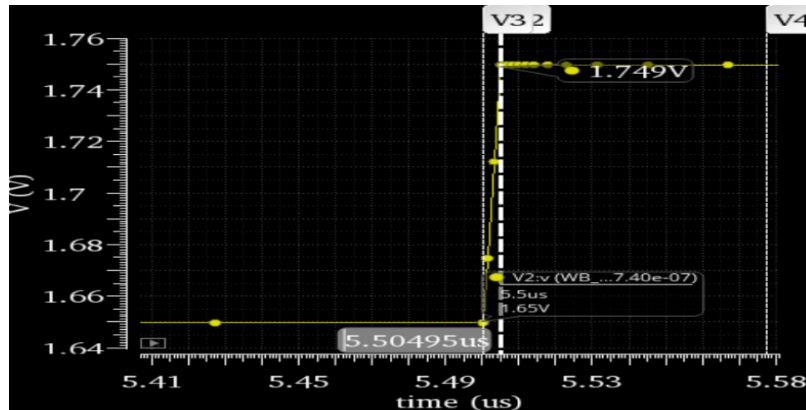


Figure 18 Vout Impulse Response

As shown in figure 18, The $FGE = \frac{V_{final,sim} - V_{expected}}{V_{expected}} = \frac{1.749 - 1.75}{1.75} = -0.057\%$

And the settling time $T_s = 5.50495 - 5.501 = 3.95 \text{ ns}$.

Hand Analysis:

$$FGE = \frac{-1}{LG} = \frac{-1}{\frac{67}{10^{20}}} * 100 = -0.045\%$$

$$1\% \text{ Settling time} = -\ln(0.01)\tau = 3.38 \text{ ns}$$

Summary

Specification	Required	Achieved
DC Gain	58dB	67.3dB
GBW	150M	163M
SR	100 V/ sec	102 V/ sec
Output Swing	1.5 V _{pp}	1.72 V _{pp}
Input referred noise	30nv/pHz	7.08nv/pHz
PM	60	78.26
GM	12	29.70
Power Consumption	min.	328.9uA (1.08mW)
Area	min.	248.45 um ²

Table 3. Achieved Specifications

It's clear that DC gain is over specification that's because the minimum length for the device is large, making it easy to achieve high gain but the cost of that is the Large Area.